

Introduction:-

- Single stage amplifiers have only one amplifying device.
- The amplification is obtained from single stage amplifier is not sufficient, so we need to connect two or more amplifying devices for large amplification.
- There are two or more amplifying devices are connected in series or cascade.
- Cascade / series is nothing but the output of one stage is connected to the input of the next stage.
- The output of each stage have large amplification i.e., large large output voltage compared to the input voltage.
- The multistage amplifier the output of the 1st stage should be coupled to the input of next stage and so on.

Classification of Amplifiers:-

Depending upon the type of coupling, the multistage amplifiers are classified as

1. RC Coupled Amplifiers
2. Transformer ^{Coupled} Amplifiers
3. Direct Coupled Amplifiers

AC Coupled Amplifier:-

In multistage AC coupled amplifier, the output of one stage is coupled to the input of the next stage by a capacitor. But in this circuit there is no separate load capacitor between collector and ground. Let R_c acts as a load resistor. AC coupled amplifier has good frequency response at low frequency. So this amplifier is widely used.

1. Transformer Coupled Amplifier:-

In this amplifier, the output of the 1st stage is coupled to the input of the next stage through Transformer. But in transformer coupling mutual gain will be increased and impedance matching will be achieved.

This type of amplifier will have low frequency response. Because inductance of transformer winding will be large. So it is used in power amplifiers.

2. Direct Coupled Amplifier:-

In this type of amplifier, the output of the 1st stage is directly coupled to the input of the next stage without any coupling device (i.e., capacitor).

In this amplifier, we get large amplification at low frequency.

→ AC coupled amplifier cannot be used for amplification of low frequency signal because X_c will tend to vary large at low freq signal. So the coupling capacitor is open ckt for low freq. signal. i.e. $X_c = \frac{1}{2\pi f C}$
if $f \rightarrow 0$ then $X_c \rightarrow \infty$

Coupled Transistor Amplifier

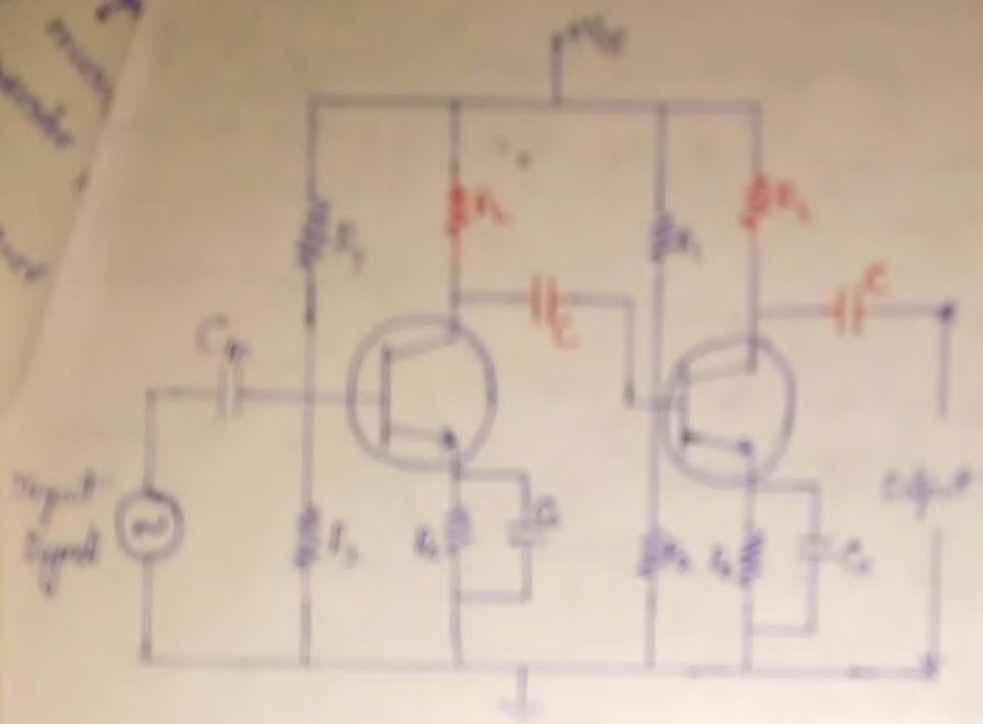


Fig. Circuit diagram of DC coupled amplifier

The above fig shows a two stage DC coupled amplifier using common emitter configuration.

The output of the first stage is coupled to the input of second stage through coupling capacitor. It is biased by a resistor network. It is used to transfer the signal & maintain its waveform.

Operation:


- The resistors R_1 , R_2 and R_3 form a biasing and stabilization network.
- The bypass capacitor C_E prevents the loss of amplification.
- The coupling capacitors are also known as blocking capacitors which block DC and allow AC voltage.

Operation:-

AC signal is applied to the base of the transistor. An amplified signal will develop across the collector of the transistor.

- the amplified signal is coupled capacitor C_c .
- the 1st stage can be used for further amplification of the signal and thus the gain increases.
- the 3rd stage is out of phase with the 1st stage and the phase signal is fed to the 2nd stage.
- therefore the overall effect of 3 stages is in phase with the 1st stage with higher amplitude.

Frequency Response:

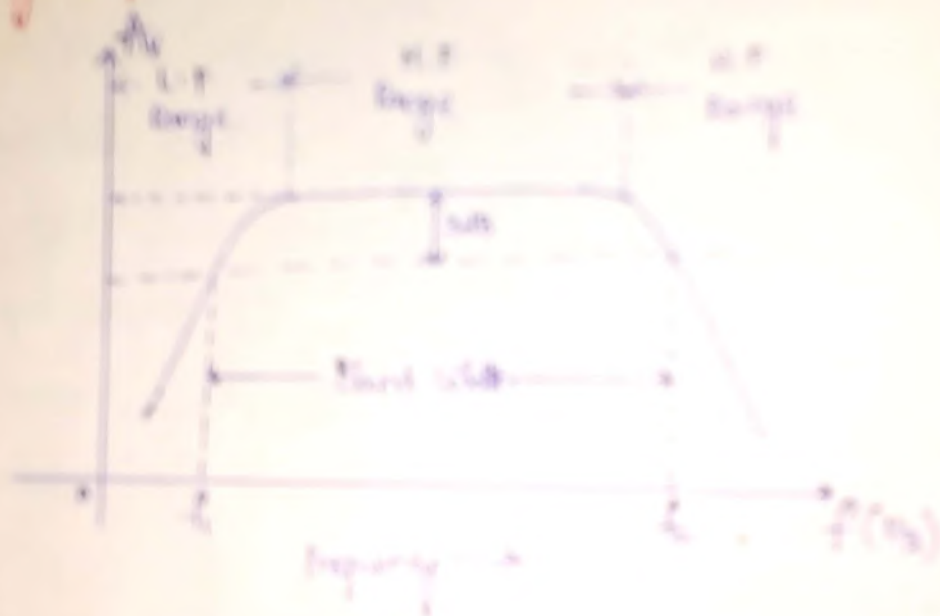

The frequency response of RC coupled amplifier

The above fig shows the freq response of RC coupled amplifier.

The freq response is the graph b/w frequency and gain.

as it is from the freq. response curve that the
voltage gain is maximum and constant at mid frequencies.
The voltage gain is low at lower and higher frequencies.
The behaviour of the freq. response is briefly explained
below.

At lower frequencies-

At low frequencies, the reactance of the coupling capacitor
will increase, the voltage gain of the circuit will
be decreased from mid range to lower range.
→ Due to large reactance, the capacitor C_c cannot pass the
the smaller voltage V_c . Due to this a factor the voltage
gain will decrease at low frequencies.

At high frequencies-

→ At high frequencies, the reactance of coupling capacitor
will be very small and is known as a short circuit
but due to junction capacitance the voltage gain will
decrease at high frequency. So the gain can be constant
at high frequencies.

At mid frequencies-

At mid frequencies, the voltage gain of the amplifier
is constant. The effect of coupling capacitor is to maintain the
uniform voltage gain at mid frequency range.

→ It has low impedance which leads to low loss at the same time.

→ It also has better almost neutral and making a uniform voltage gain at all frequencies.

Advantages:-

→ It provides a good freq. response.

→ It has low expense.

→ It is a small size.

→ It has low weight and low complexity.

Disadvantages:-

It provides poor impedance matching.

Applications:-

It is used in

1. Radio Receiver

2. Tape Recorder


3. TV Receiver.

→ It is a good example of independent of frequency where the freq. range has become so wide that it has become independent of frequency.

- Amplifiers -

If two or more stages may be connected in cascade when the stage amplification is not sufficient for particular purpose amplification when the β and r_{in} of input is not satisfying the circuit applications.

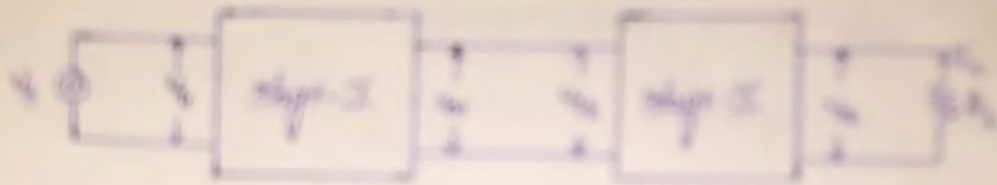
Cascade amplifier stages is shown in below fig.



Let us consider two stage cascaded amplifier. The 1st stage is connected in CC configuration. If 2nd stage is connected in CC configuration. It cannot give a high β at 1st stage and 2nd stage provides high input impedance & low r_{out} .

To get β_{in} , r_{in} , β_{out} & r_{out} expressions we must take the parameters of in each particular.

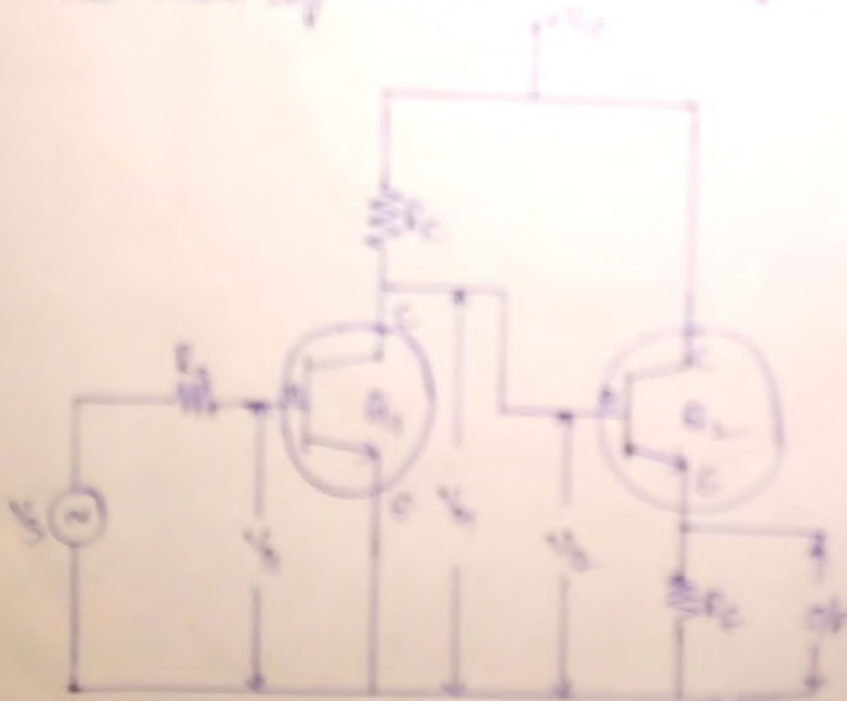The below fig. shows the two stage cascaded amplifier.



- The above circuit shows that two stages
- The transistor Q_1 is in first stage and
- is in 2^{nd} stage.
- The transistor Q_2 is in CC configuration, and
- is in CC configuration.
- The V_{B1} is bias for the emitter terminal of Q_1 ,
there is no separate bias network of 1st stage, as it
is also as a load network.
- The ac equivalent circuit for the above circuit is in
in below fig.



Fig. AC equivalent circuit for cascading amplifier.

2. Gain above which limiting networks are not shown since that is not only to provide the proper operating point & they do not affect the response of the amplifier.

3. The ratio V_1 is the 1st stage & V_2 is the 2nd stage. So the overall voltage gain is defined as the ratio of 1st stage of 2nd stage to the voltage of 1st stage.

$$A_{V1} = \frac{V_{o1}}{V_i}$$

$$A_{V2} = \frac{V_{o2}}{V_{o1}} = \frac{V_{o2}}{V_{i1}}$$

$$A_{V3} = \frac{V_{o3}}{V_{i2}} = \frac{V_{o3}}{V_{o1}}$$

$$A_{V4} = A_{V1} \cdot \frac{V_{o1}}{V_i}$$

we know that $V_{i1} = V_i$ $\therefore A_{V4} = A_{V1} \cdot \frac{V_{o1}}{V_i}$

$$\therefore A_{V4} = A_{V1} \cdot A_{V2} \cdot A_{V3}$$

Band Width:-

Band width is defined as the difference b/w upper cut off freq and lower cut off freq.


$$\therefore BW = f_2 - f_1$$

where f_1 & f_2 are the cut off freqs.

$\rightarrow A_V$ is max value of gain obtained from the frequency response characteristic.

$\rightarrow$ Gain at cut off freq is f_1 or $f_2 = \frac{A_V}{\sqrt{2}}$

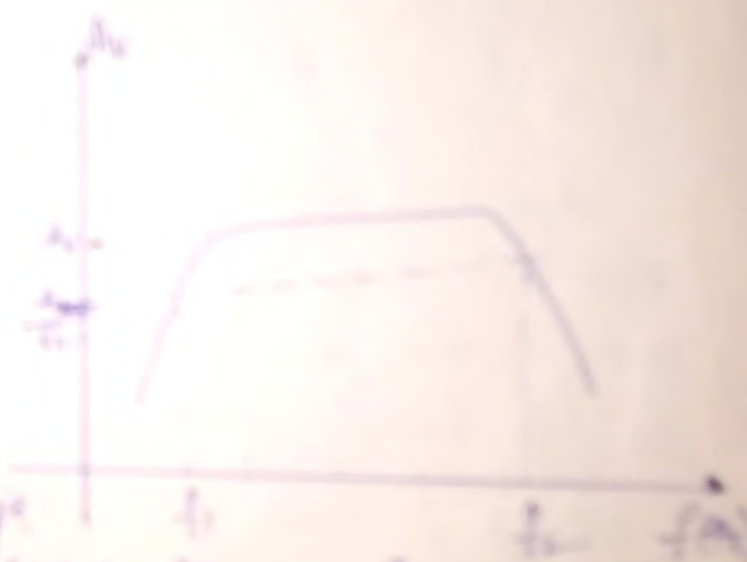$\rightarrow$ The calculation of gain is done with the help of voltage divider.



→ let us consider the mid
range gain in dB = $20 \log A_v$

$$A_v = 100$$

$$A_v = 20 \log 10$$

$$A_v = -20 \text{ dB}$$

$$A_v = 20 \log 100$$

$$A_v = 40 \text{ dB}$$

→ In a single stage amplifier, the voltage gain in the high frequency region of the frequency response characteristic of an amplifier is given by the following eq assuming the resonant mid band gain of the amplifier to be unity.

$$A_{vm} = \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

where f_{vm} denotes the voltage gain in the resonant amplifier. So f_{vm} is the gain of the 1 stage or ~~high~~ high frequency region. So that f_{vm} is the gain of the n amplifier stages in the high frequency region.

Similarly f_c is the upper cut off freq.

$$f_c = f_{c1} \cdot f_{c2} \cdot f_{c3} \dots f_{cn}$$

→ let us consider the upper cut off freq of n identical stages as f_{cn} . It is the freq for which the overall gain falls to 0.707 of the mid band value.

$$\left[\sqrt{1 + \left(\frac{f_c}{f} \right)^2} \right]^n = \frac{1}{A_v}$$

If f_c is the upper cut-off
 $\left(\frac{f_c}{f} \right)^2 = \frac{1}{A_v^2} - 1$ for $f = f_c$

$$\left[\sqrt{1 + \left(\frac{f_c}{f} \right)^2} \right]^n = \frac{1}{A_v}$$

f_c is the frequency at which
 $A_v = \frac{1}{\sqrt{2}}$

$$\left(\sqrt{1 + \left(\frac{f_c}{f} \right)^2} \right)^n = \frac{1}{A_v}$$

Taking square on both sides

$$\left(1 + \left(\frac{f_c}{f} \right)^2 \right)^n = \frac{1}{A_v^2}$$

Taking n^{th} root on both sides.

$$1 + \left(\frac{f_c}{f} \right)^2 = \frac{1}{A_v^{2/n}}$$

$$\left(\frac{f_c}{f} \right)^2 = \frac{1}{A_v^{2/n}} - 1$$

$$\frac{f_c}{f} = \sqrt{\frac{1}{A_v^{2/n}} - 1}$$

$$f_c = f \sqrt{\frac{1}{A_v^{2/n}} - 1}$$

In a single stage amplifier, the voltage gain is frequency
 response characteristic of an amplifier is given by following
 eq. Assuming that the reactances will have gain to be unity.

$$A_v = \frac{1}{\sqrt{1 + \left(\frac{f_c}{f} \right)^2}}$$

f_0 is given of 1st degree component

f_1 is 2nd of component degree

f_2 is 3rd given of 1st component degree

$f_3, f_4, f_5, \dots, f_n$

Let us consider least sq frequency of an n component
observed steps as f_n . It is the best response for which
error given falls in the of the observed value.

$$\left[\sqrt{n} \left(\frac{f_n}{f_0} \right) \right]^2 = \frac{1}{f_0^2}$$

$$f_0 = \left[\sqrt{n} \left(\frac{f_n}{f_0} \right) \right]^2$$

$$f_0 = \left[\sqrt{n} \left(\frac{f_n}{f_0} \right) \right]^2$$

$$f_0^3 = n \left(\frac{f_n}{f_0} \right)^2$$

$$\sqrt{f_0^3} = \left(\frac{f_n}{f_0} \right)^2$$

$$\therefore f_0 = \frac{f_n}{\sqrt{f_0^3}}$$

Bandwidth product:-

Gain Bandwidth product is referred as figure of merit. It is used to measure the performance of an amplifier.

→ Any amplifier circuit must have high gain and large Bandwidth.

→ In certain amplifier circuit, without gain may be large but not bandwidth and vice versa.

→ Different amplifier circuits can be compared with this parameter, the expression for gain bandwidth product of BJT

$$A \cdot f_c = f_T = \frac{g_m}{2\pi C_c} = \frac{1}{2\pi C_c}$$

where C_c - circuit Capacitor

At $f = f_c$ Current gain, $A_v = 1$

∴, value of gain bandwidth product is f_T itself
for high frequency amplifier as expression for f_T is

$$f_T = \frac{g_m}{2\pi C_c}$$

Decibel:-

It is convenient to compare the powers on a logarithmic scale rather than on a linear scale. The unit of this logarithmic scale is called the decibel abbreviated as db.

Suppose P_2 is the output power & P_1 is the input power, then the gain in decibel is

$$N = 10 \log \frac{P_2}{P_1}$$

If 'A' is normal voltage gain $A_v = \frac{V_2}{V_1}$

Decibel voltage gain $A' = 20 \log A$

If R_1 is i/p Resistance, Input power, $P_1 = \frac{V_1^2}{R_1}$

If R_2 is o/p Resistance, Output power $P_2 = \frac{V_2^2}{R_2}$

$$\therefore \text{power gain } G = \frac{P_2}{P_1} = \frac{V_2^2 \cdot R_1}{V_1^2 \cdot R_2}$$

If the impedances are matched, i.e. input resistance $R_1 = \text{o/p } R_2$


$$\text{power gain } G = \frac{V_2^2}{V_1^2} = A^2$$

$$\begin{aligned} \text{In db's } 10 \log G &= 10 \log A^2 \\ &= 20 \log A. \end{aligned}$$

the analysis of C.C coupled amplifier, the following simplifying assumptions are made:

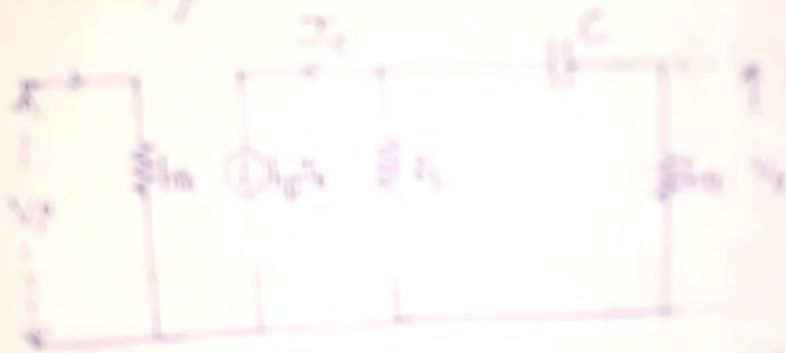- (1) R_{in} is so small that an average source load can be neglected.
- (2) R_{out} is so large and it can be considered as an open circuit.
- (3) The reactance of C_c for any given input frequency is so small that the parallel combination of R_{in} and C_c can be effectively considered as a short circuit.
- (4) The time constants τ_1 and τ_2 are usually large as compared to t_{in} .


With these assumptions, the simplified equivalent circuit is shown in fig.




The simplified equivalent circuit of C.C. coupled amplifier

Mid-frequency range:-

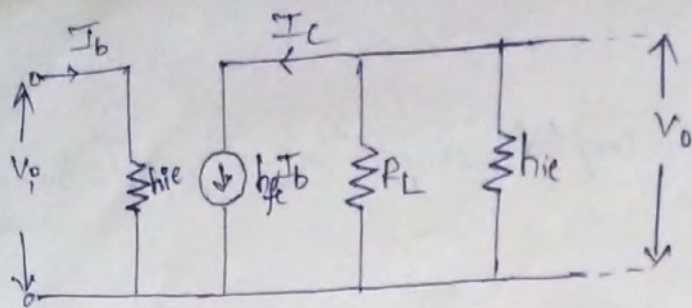At mid-frequencies, the impedances offered by coupling capacitors C_c is so small as to be an effective short circuit. Thus at mid-frequencies, the effect of coupling capacitors C_c can be neglected. Now the equivalent circuit is shown in fig. (c). The Thevenin equivalent circuit is shown in fig. (c).



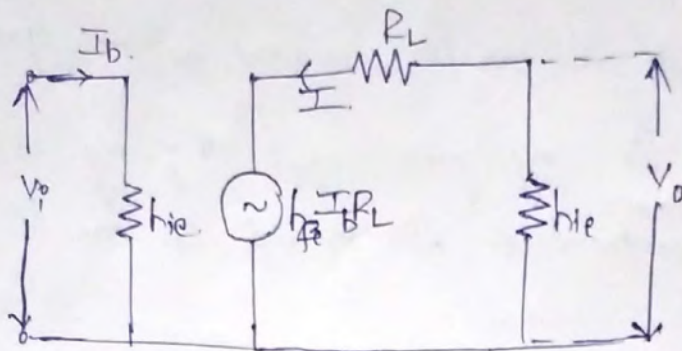① Equivalent circuit at mid frequency range



② Thevenin's equivalent circuit.

From fig ②.
$$I = \frac{-h_{fe} I_b R_L}{R_L + h_{ie}} \longrightarrow (1)$$

$\therefore$ Current gain $(A_i)_m = \frac{I}{I_b} = -\frac{h_{fe} R_L}{R_L + h_{ie}} \longrightarrow (2)$

The magnitude of current gain is given by.

$$|(A_i)_m| = \frac{h_{fe} R_L}{R_L + h_{ie}} \longrightarrow (3)$$

The output voltage $V_o = h_{fe} I_c$.

$$= -\frac{h_{ie} h_{fe} I_b R_L}{R_L + h_{ie}} \longrightarrow (4)$$

The input voltage

$$V_o = h_{ie} I_b \longrightarrow (5)$$

$$V_o = -\frac{h_{ie} h_{fe} I_b R_L}{R_L + h_{ie}}$$

$$\therefore \text{Voltage gain } (A_v)_m = \frac{V_o}{V_i} = -\frac{h_{fe} R_L}{R_L + h_{ie}} \rightarrow (8)$$


The magnitude of voltage gain at mid frequency is given by

$$|(A_v)_m| = \frac{h_{fe} R_L}{h_{ie} + R_L}$$


The negative sign shows the phase angle of 180° . It is obvious from eq (2) & eq (8) that $(A_i)_m = (A_v)_m$.

Low frequency range:-

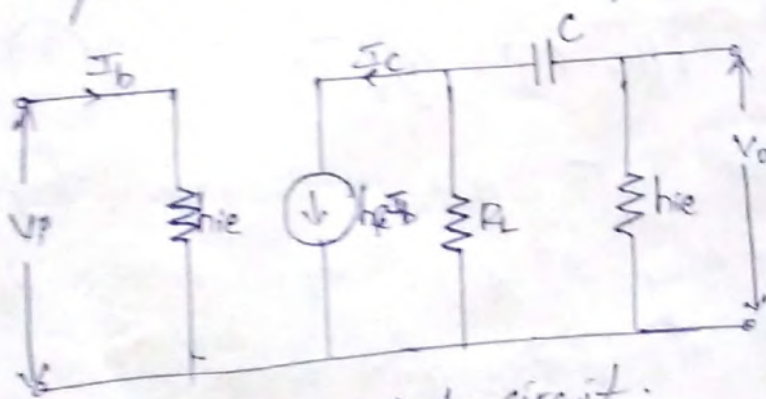In low frequency range the impedance offered by coupling capacitor is comparable to the load resistance. Hence it largely affects current amplification. Therefore, it is included in their equivalent circuit. The equivalent circuit is shown in fig (a). fig (b) represents the Thevenin equivalent circuit.



(a) Equivalent circuit.

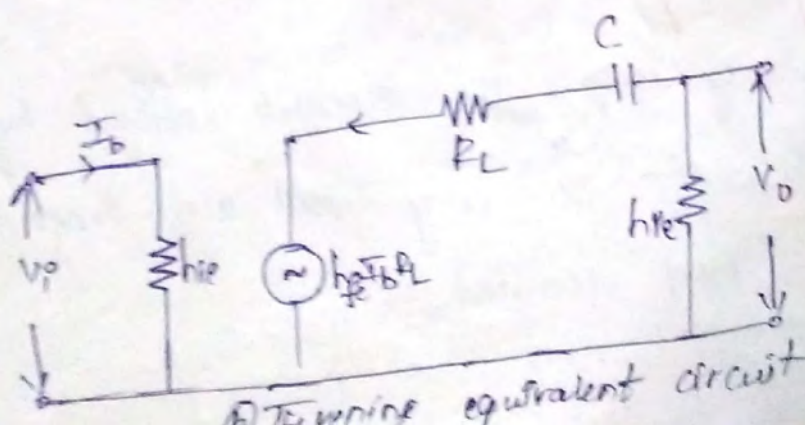

(b) Thevenin equivalent circuit

Fig: Equivalent circuit at low frequency range

The current flowing in the circuit

$$I = \frac{-h_{fe} I_b R_L}{h_{ie} + R_L - j/\omega C}$$

The current gain at low frequencies is given

$$(A_i)_1 = \frac{I}{I_b} = \frac{-h_{fe} R_L}{h_{ie} + R_L - j/\omega C}$$

Output voltage $V_o = \text{Resistance} \times \text{Current}$

$$\therefore V_o = h_{ie} \times \frac{-h_{fe} I_b R_L}{h_{ie} + R_L - j/\omega C} = \frac{-h_{fe} h_{ie} I_b R_L}{h_{ie} + R_L - j/\omega C}$$

Input voltage $V_p = h_{ie} \times I_b$

$$\therefore (A_v)_1 = \frac{V_o}{V_p} = \frac{-h_{fe} R_L}{h_{ie} + R_L - j/\omega C}$$

The magnitude of $(A_v)_1$ is given by

$$(A_v)_1 = \frac{h_{fe} R_L}{\sqrt{(h_{ie} + R_L)^2 + (1/2\pi f C)^2}} \longrightarrow (7)$$

It is obvious from eq (7) that in the low frequency range, as the frequency f of the input voltage decreases, the magnitude of the voltage gain decreases.


High Frequency range:

① In high frequency range, the reactance offered by coupling capacitor 'C' is very small and hence it can be considered as short circuited.


In a bipolar transistor, there are two depletion regions across two PN junctions. They behave like a dielectric media and hence give rise to two internal capacitances. At high frequency range the reactance of these capacitances (C_{be} & C_{bc}) considered.

The C_{be} and C_{bc} may be replaced with a single capacitance C_d across the input resistance h_{ie} of the transistor.

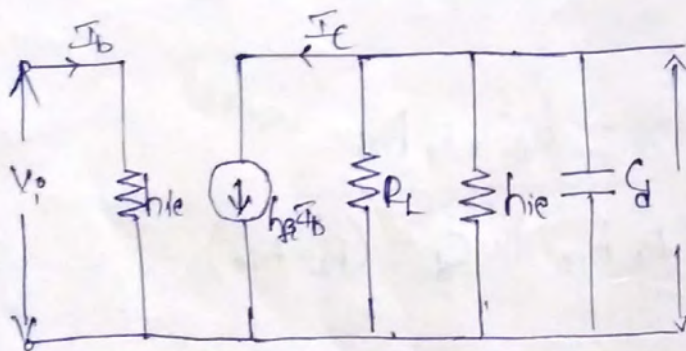- (iii) The value of shunt capacitance C_d in the input circuit of the first stage is small because it depends on the df impedance of the first transistor. But in the output circuit of the first stage C_d is increased by stray capacitance of the wiring. Therefore, the reactance $1/\omega C_d$ will have appreciable shunting effect on R_L and h_{ie} .
The equivalent ckt's are shown in fig (a) & fig (b).



(a) Equivalent ckt at high frequencies.

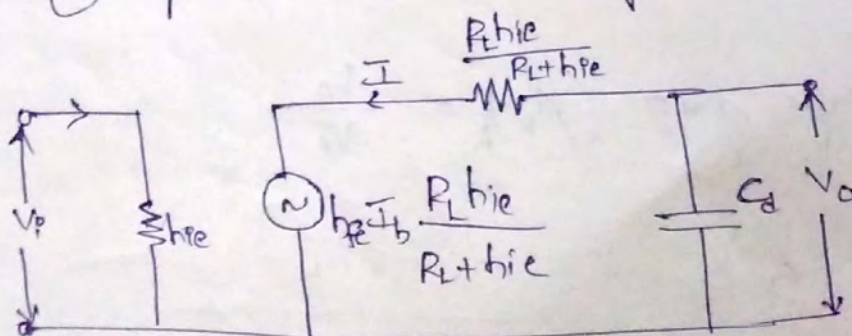

(b) Thevenin equivalent circuit.

Current flowing in the circuit is given by

$$I = \frac{-h_{fe} I_b \frac{R_L h_{ie}}{R_L + h_{ie}}}{\frac{R_L h_{ie}}{R_L + h_{ie}} + \frac{1}{j\omega C_d}} = \frac{-h_{fe} I_b R_L h_{ie}}{R_L h_{ie} + \frac{1}{j\omega C_d} (R_L + h_{ie})}$$

$$\therefore \text{Current gain } (A_i)_h = \frac{I}{I_b} = \frac{-h_{fe} h_{ie} R_L}{R_L h_{ie} + \frac{1}{j\omega C_d} (R_L + h_{ie})}$$

Output voltage $V_o = I \times \frac{1}{j\omega C_d}$

$$V_o = \frac{-h_{fe} I_b R_L h_{ie} / (R_L + h_{ie})}{\left[(R_L h_{ie}) / (R_L + h_{ie}) + \frac{1}{j\omega C_d} \right]} \times \frac{1}{j\omega C_d}$$

$$= \frac{-h_{fe} I_b R_L h_{ie}}{R_L h_{ie} j\omega C_d + (R_L + h_{ie})}$$

Input voltage $V_i = I_b h_{ie}$

$$\therefore \text{Voltage gain } (A_v)_h = \frac{V_o}{V_i}$$

$$(A_v)_h = \frac{-h_{fe} R_L}{1 + j\omega C_d (R_L + h_{ie})}$$