

INTRODUCTION


POWER SYSTEM ANALYSIS:-

1. Evaluation of power system is called power system analysis i.e. studying the characteristics or behaviours.
2. Basically power system consists of generation system, transmission and distribution system.
3. The main characteristics of power system is it neither generate the energy nor store the energy.

Function of power system:-

1. To design a new system and also to design a future expansion of existing power system.
2. To analyse the stability of system when it is subjected large and small disturbance.
3. To design the circuit breaker for various power condition.

Modern Power System:-

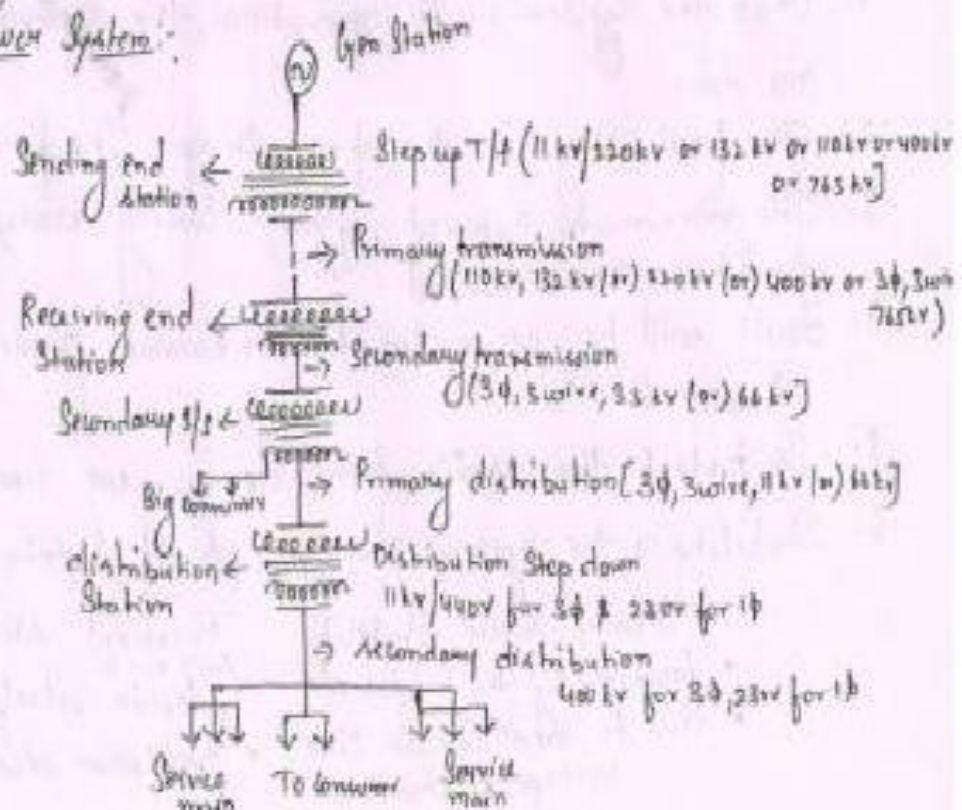

Sub:

Sub. Code:

Year/Sem:

Unit No.:

Session No.: 02

Date:

Analysis for System planning and Operational Studies:-Normal Condition:-

Uninterrupted power + reliable or constant power

$$\text{Generation} = \text{Demand}$$

SYSTEM PLANNING:-

1. To fulfill the demand, generation should be greater than the demand.
2. The transmission parameters due to be calculated
3. Voltage through transmission lines is proportional to the reactive power $V \propto Q$
4. This is studied via power flow through transmission lines.
5. Capacitor is used for boost up the voltage.

OPERATIONAL STUDIES:-


1. Once the system is in operation, the Operational Studies are done.
2. The first stage is the fault Study. The faults are studied.
3. The maximum current flow during various faults condition are studied.
4. Fault will be occur due to unbalance current is flow through it.
5. To protect the device from damage we use circuit breaker.
6. Stability of the System can be classified into

<u>Steady state Stability</u> * gained by the system * due to small fault like voltage fluctuation	<u>Transient Stability</u> can't able to * regain itself by system * breakdown due to large faults.
--	--


Sub:
Sub. Code:
Year/Sem:

Unit No.:
Session No.: 03 & 04
Date:

Basic Components of a power system:-

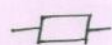Generator - (G), Two winding power T/f - 
3-winding T/f - , Transmission - 
C.B - , Loads 
C.T - , P.T - 

Single line diagram:-

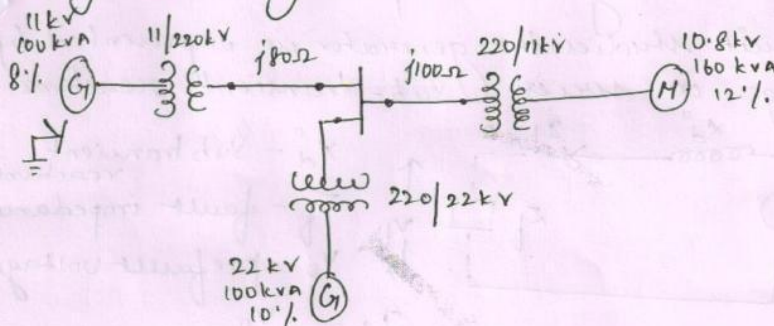

Modelling of power system components:-

1. Generator modelling
2. Transformer modelling
3. Transmission line modelling
4. Load modelling.

Sub:

Sub. Code:

Year/Sem:


Unit No.:

Session No.:

Date:

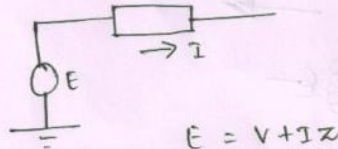
1. Modelling of generators:-

For power flow studies synchronous generator is represented by its generated voltage in series Thevenin's impedance




$Z \rightarrow$ steady state impedance

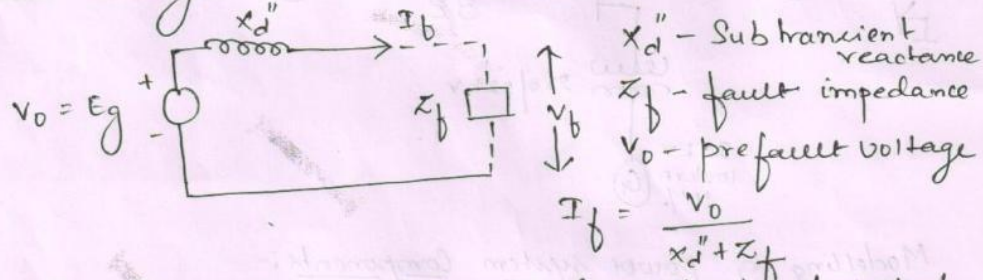For short circuit studies the generator is represented by prefault voltage in series sub-transient reactance



For the transient stability studies during transient period the damper winding has high resistance and this component of current leakage quickly.

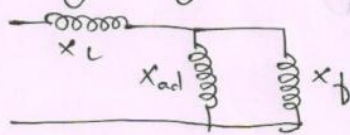$\therefore$ Neglecting damper winding we have




Short ckt transient reactance

$$x_d' = x_L + \left[\frac{1}{x_{ad}} + \frac{1}{x_f} \right]^{-1}$$

Sub:
Sub. Code:
Year/Sem:


Unit No.:
Session No.:
Date:

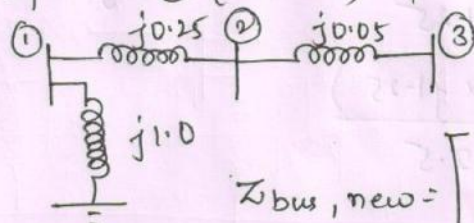Step ③ :- Addition of a branch of impedance $z = j0.05$ b/w bus ② (old bus) & bus ③ (new bus)



$$Z_{bus, new} = \begin{bmatrix} j1.0 & j1.0 & j1.0 \\ j1.0 & j1.25 & j1.25 \\ j1.0 & j1.25 & j1.25 + j0.05 \\ & & = j1.3 \end{bmatrix}$$

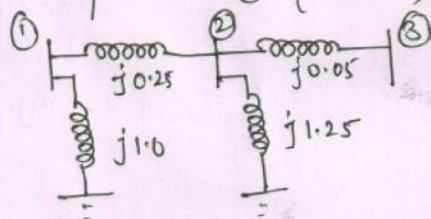Step ④ :- Addition of a branch of impedance $z = j1.25$ b/w bus ① (old bus) & ref bus.



$$Z_{bus, new} = \begin{bmatrix} j1.0 & j1.0 & j1.0 & j1.0 \\ j1.0 & j1.25 & j1.25 & j1.25 \\ j1.0 & j1.25 & j1.3 & j1.25 \\ j1.0 & j1.25 & j1.25 & j1.25 + j1.25 \\ & & & = j2.5 \end{bmatrix}$$

$$Z_{jk, new} = Z_{jk, old} - \frac{Z_{in} \times Z_{nk}}{Z_{nn}}$$

$$Z_{11} = j1.0 - \frac{j1.0 \times j1.0}{j2.5}, \quad \boxed{Z_{11} = j0.6}$$

$$Z_{12} = j1.0 - \frac{j1.0 \times j1.25}{j2.5}, \quad \boxed{Z_{12} = j0.5}$$


$$Z_{13} = j1.0 - \frac{j1.0 \times j1.25}{j2.5}, \quad \boxed{Z_{13} = j0.5}$$

Sub:
Sub. Code:
Year/Sem:

Unit No.:
Session No.: 11
Date:

Z-bus building algorithm

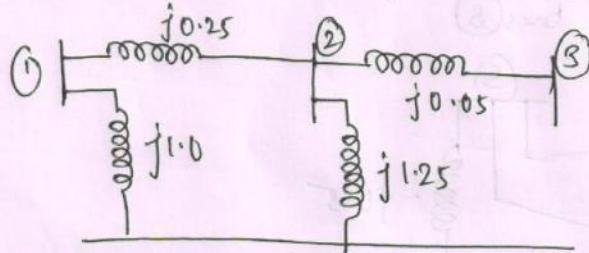Formation Z-bus has Z-bus building Algorithm:-



Formation of Z-bus by using Z-bus building Algorithm involves 4 steps

Step ①:- Adding a branch of impedance Z b/w ref bus & the new bus.


Step ②:- Adding a branch of impedance Z b/w old bus & the new bus.

Step ③:- Adding a branch of impedance Z b/w old bus & the ref bus.

Step ④:- Adding a branch of impedance Z b/w two existing buses


Step ①:- Addition of a branch of impedance $Z = j1.0$ b/w ref bus & bus ① (new bus)

$$Z_{bus, new} = [j1.0]$$

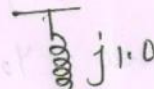

Step ②:- Addition of a branch of impedance $Z = j0.25$ b/w bus ① (old bus) & bus ② (new bus)

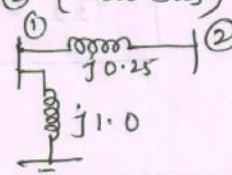
$$\therefore Z_{bus, new} = \begin{bmatrix} j1.0 & j1.0 \\ j1.0 & j1.0 + j0.25 \\ & & j1.25 \end{bmatrix}$$



Sub:
Sub. Code:
Year/Sem:


Unit No.:
Session No.:
Date:

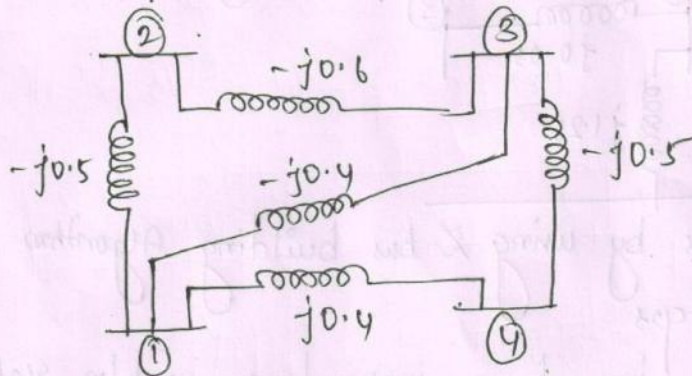1. For the below network determine the new admittance matrix when a branch of admittance $j0.2$ is added b/w bus ② & bus ③



$$Y_{bus} = \begin{bmatrix} -j1.3 & j0.5 & j0.4 & j0.4 \\ j0.5 & -j1.1 & j0.6 & 0 \\ j0.4 & j0.6 & -j1.5 & j0.5 \\ j0.4 & 0 & j0.5 & -j0.9 \end{bmatrix}$$

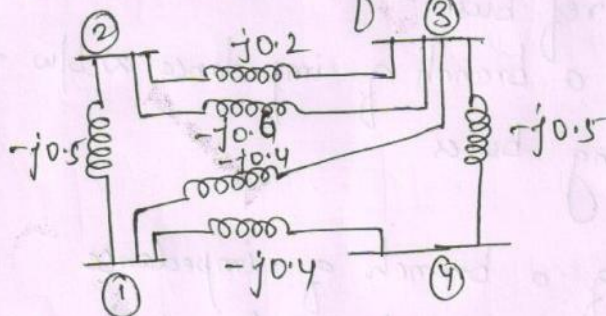Add a branch of admittance in b/w bus ② & ③



$$Y_{ii, new} = Y_{ii, old} + y$$

$$Y_{22, new} = Y_{22, old} + y$$

$$Y_{22, new} = (-j1.1) + (j0.2)$$

$$Y_{22} = -j0.9$$

$$Y_{33, new} = Y_{33, old} + y$$

$$Y_{33, new} = (-j0.15) + (j0.2)$$

$$Y_{33} = -j1.3$$

$$Y_{ij, new} = Y_{ij, old} - y$$

$$= j0.6 - j0.2$$

$$Y_{23} = j0.4$$

$$Y_{32} = Y_{23} = j0.4$$

$$Y_{bus} = \begin{bmatrix} -j1.3 & j0.5 & j0.4 & j0.4 \\ j0.5 & -j0.9 & j0.4 & 0 \\ j0.4 & j0.4 & -j1.3 & j0.5 \\ j0.4 & 0 & j0.5 & -j0.9 \end{bmatrix}$$

Formula:-

To calculate the admittance when an element of an admittance y is added or remove from the network

i) Addition of element b/w bus i & j

$$Y_{ii, \text{new}} = Y_{ii, \text{old}} + y$$

$$Y_{jj, \text{new}} = Y_{jj, \text{old}} + y$$

$$Y_{ij, \text{new}} = Y_{ij, \text{old}} - y$$

ii) Removal of element b/w bus i & j

$$Y_{ii, \text{new}} = Y_{ii, \text{old}} - y$$

$$Y_{jj, \text{new}} = Y_{jj, \text{old}} - y$$

$$Y_{ij, \text{new}} = Y_{ij, \text{old}} + y$$

iii) Addition of Shunt element at bus i

$$Y_{ii, \text{new}} = Y_{ii, \text{old}} + y$$

Sub:
Sub. Code:
Year/Sem:

Unit No.:
Session No.:
Date:

$$Y_{11, \text{new}} = -j1.3 - \frac{j0.4 \times j0.4}{-j0.9} = -j1.12, \quad Y_{11, \text{new}} = -j1.12$$

$$Y_{12, \text{new}} = j0.5 - \frac{j0.4 \times 0}{-j0.9} = j0.5, \quad Y_{12, \text{new}} = j0.5$$

$$Y_{13, \text{new}} = j0.4 - \frac{j0.4 \times j0.5}{-j0.9} = j0.6, \quad Y_{13, \text{new}} = j0.6$$

$$Y_{21, \text{new}} = Y_{12, \text{new}} = j0.5$$

$$Y_{22, \text{new}} = -j1.1 - \frac{0 \times 0}{-j0.9} = -j1.1, \quad Y_{22, \text{new}} = -j1.1$$

$$Y_{23, \text{new}} = j0.6 - \frac{0 \times j0.5}{-j0.9} = j0.6, \quad Y_{23, \text{new}} = j0.6$$

$$Y_{31, \text{new}} = Y_{13, \text{new}} = j0.6$$

$$Y_{32} = j0.6$$

$$Y_{33} = -j1.5 - \frac{j0.5 \times j0.5}{-j0.9} = -j1.22$$

$$Y_{33} = -j1.22$$

$$Y_{\text{bus}} = \begin{bmatrix} -j1.12 & j0.5 & j0.6 \\ j0.5 & -j1.1 & j0.6 \\ j0.6 & j0.6 & -j1.22 \end{bmatrix}$$

Sub:

Sub. Code:

Year/Sem:

Unit No.:

Session No.:

Date:

$$Y_{41} = -Y_{14} = 0$$

$$Y_{42} = -Y_{24}$$


$$Y_{42} = -0.24 + j0.94$$

$$Y_{43} = -0.29 + j1.18$$

$$Y_{44} = 0.49 - j2.24$$

$$Y_{bus} = \begin{bmatrix} 0.88 + j3.53 & -0.29 + j1.17 & -0.59 + j2.33 & 0 \\ -0.29 + j1.17 & 0.86 - j3.2 & -0.33 + j & -0.24 + j0.94 \\ -0.59 + j2.33 & 0.33 + j & 1.21 - j4.65 & -0.29 + j1.18 \\ 0 & -0.24 + j0.94 & -0.29 + j1.18 & 0.49 - j2.14 \end{bmatrix}$$

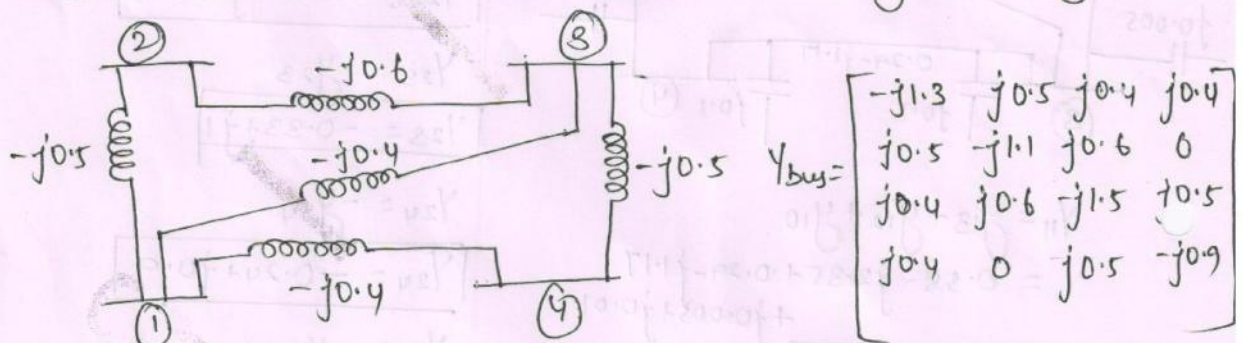3. Determine the bus admittance shown below.
Determine the reduced admittance matrix by eliminating node 4.



To find the element of reduced admittance matrix

$$Y_{jk, \text{new}} = Y_{jk, \text{old}} - \frac{Y_{jn} \times Y_{nk}}{Y_{nn}}$$

$n \rightarrow$ node to be eliminate

$$Y_{jk, \text{new}} = Y_{jk, \text{old}} - \frac{Y_{j4} \times Y_{4k}}{Y_{44}}$$


$$\begin{aligned} n &= 4 \\ j &= 1, 2, 3 \\ k &= 1, 2, 3 \end{aligned}$$

Sub:
Sub. Code:
Year/Sem:

Unit No.:
Session No.:
Date:

2. The parameter of a four bus is shown below

line	line impedance	line charging admittance	line admittance
1-2	$0.2 + j0.8$	$j0.02$	$0.29 - j1.17$
2-3	$0.3 + j0.9$	$j0.03$	$0.33 - j1$
2-4	$0.25 + j1.0$	$j0.04$	$0.24 - j0.94$
3-4	$0.2 + j0.8$	$j0.2$	$0.29 - j1.17$
1-3	$0.1 + j0.4$	$j0.01$	$0.58 - j2.35$

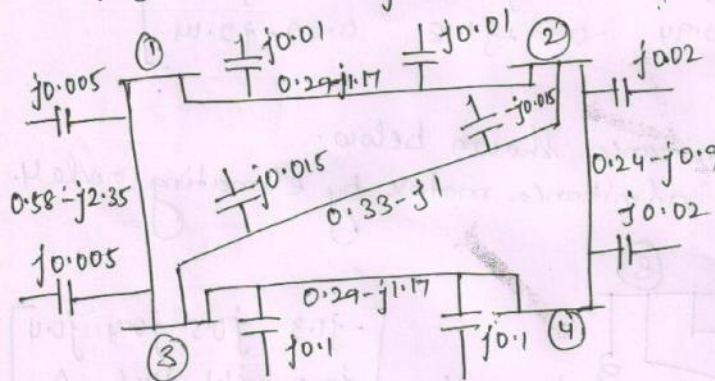

$$Y_{11} = Y_{13} + Y_{12} + Y_{10}$$

$$= 0.58 - j2.35 + 0.29 - j1.17 + j0.005 + j0.01$$

$$Y_{11} = 0.87 - j3.5$$

$$Y_{12} = -Y_{21}$$

$$Y_{12} = -0.29 + j1.17$$

$$Y_{13} = -Y_{31}$$

$$Y_{13} = -0.58 + j2.35$$

$$Y_{14} = -Y_{41}$$

$$Y_{14} = 0$$

$$Y_{21} = -Y_{12}$$

$$Y_{21} = -0.29 + j1.17$$

$$Y_{22} = Y_{21} + Y_{23} + Y_{24} + Y_{20}$$

$$Y_{22} = 0.86 - j3.025$$

$$Y_{23} = -Y_{32}$$

$$Y_{23} = -0.33 + j1$$

$$Y_{24} = -Y_{42}$$

$$Y_{24} = -0.24 + j0.94$$

$$Y_{31} = -Y_{13}$$

$$Y_{31} = -0.58 + j2.35$$

$$Y_{32} = -Y_{23}$$

$$Y_{32} = 0.33 - j1$$

$$Y_{33} = 1.21 - j4.65$$

$$Y_{34} = -Y_{43}$$

$$Y_{34} = -0.29 + j1.17$$

Sub:


Sub. Code:

Year/Sem:

Unit No.:

Session No.:

Date:

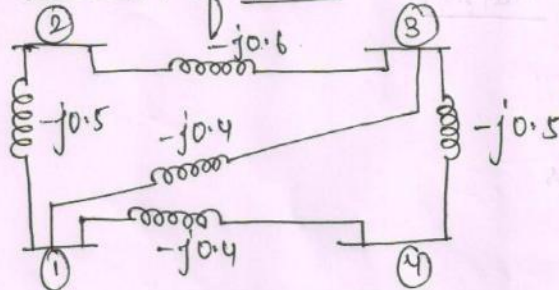Formation of Y_{bus} :-

$$Y_{11} = Y_{12} + Y_{13} + Y_{14}$$

$$= -j0.5 + (-j0.4) + (-j0.4)$$

$$Y_{11} = -j1.3$$

$$Y_{12} = -(Y_{12})$$

$$Y_{12} = j0.5$$

$$Y_{13} = -Y_{13}$$

$$Y_{13} = j0.4$$

$$Y_{14} = -(Y_{14})$$

$$Y_{14} = -j0.4$$

$$Y_{21} = -(Y_{21})$$

$$Y_{21} = j0.5$$

$$Y_{22} = Y_{21} + Y_{23} + Y_{24}$$

$$= -j0.5 + (-j0.6) + (0)$$

$$Y_{22} = -j1.1$$

$$Y_{23} = -Y_{23}$$

$$Y_{23} = j0.6$$

$$Y_{24} = -Y_{24}$$

$$Y_{24} = 0$$

$$Y_{31} = -Y_{31}$$

$$Y_{31} = j0.4$$

$$Y_{32} = -Y_{32}$$

$$Y_{32} = j0.6$$

$$Y_{33} = Y_{31} + Y_{32} + Y_{34}$$

$$= -j0.4 + (-j0.6) + (-j0.5)$$

$$Y_{33} = -j1.5$$

$$Y_{34} = j0.5$$

$$Y_{41} = j0.4$$

$$Y_{42} = 0$$

$$Y_{43} = j0.5$$

$$Y_{44} = -j0.9$$

$$Y_{Bus} = \begin{bmatrix} -j1.3 & j0.5 & j0.4 & j0.4 \\ j0.5 & -j1.1 & j0.6 & 0 \\ j0.4 & j0.6 & -j1.5 & j0.5 \\ j0.4 & 0 & -j0.5 & -j0.9 \end{bmatrix}$$

Sub:

Sub. Code:

Year/Sem:

Unit No.:

Session No.: 09

Date:

Formation of Y_{bus} Matrix:-

$$Z = R + jx$$

Y — admittances

$$Y = 1/Z$$

$$Y = 1/R + jx$$

$$\frac{1}{R} = G, \quad \frac{1}{x} = B$$

$$Y = G + jB$$

$$\frac{1}{x} = B - \text{Susceptance}$$

$$\frac{1}{R} = G - \text{Conductance}$$

$$x - \text{Reactance}$$

Bus:-

1. Meeting point of 2 or more branches
2. Conductor made up of Cu or Al
3. Voltage is constant
4. frequency is constant

Sub:

Sub. Code:

Year/Sem:

Unit No.:

Session No.:

Date:

Let load is series connected

$$Z_{pu} = R_{pu} + jX_{pu}$$

$$R_{pu} = V_{pu}^2 \cdot S_b \cdot \frac{P}{P^2 + Q^2}$$

$$X_{pu} = V_{pu}^2 \cdot S_b \cdot \frac{Q}{P^2 + Q^2}$$

$$V_{pu} = \frac{V}{V_b} = \frac{11}{11} = 1 \text{ pu}$$

$$S_b = 20 \text{ MVA}$$

$$\cos \theta = P/S \Rightarrow P = S \cos \theta = 5 \times 0.8 = 4$$

$$\sin \theta = Q/S \Rightarrow Q = S \sin \theta = 5 \times 0.6 = 3$$

$$R_{pu} = 1^2 \cdot 20 \cdot \frac{4}{4^2 + 3^2} = 3.2 \text{ pu}$$

$$X_{pu} = 1^2 \cdot 20 \cdot \frac{3}{4^2 + 3^2} = 2.4 \text{ pu}$$

$$Z_{pu} = (3.2 + j2.4)$$

Sub:
Sub. Code:
Year/Sem:

Unit No.:
Session No.:
Date:

Transformer, T₁:-

$$kV_{b \text{ new}} = kV_{b \text{ old}} \times \frac{LV}{HV}$$

$$= 132 \times \frac{12.5}{132}$$

$$kV_{b \text{ new}} = 12.5 \text{ kV}$$

$$Z_{pu, T_1} = 0.1 \times \left(\frac{20}{25}\right) \times \left(\frac{12.5}{12.5}\right)^2$$

$$Z_{pu, T_1} = j0.08 \text{ pu}$$

Generator, G₁

$$Z_{pu, G_1} = 0.15 \times \left(\frac{20}{20}\right) \times \left(\frac{11}{12.5}\right)^2$$

$$Z_{pu, G_1} = j0.116 \text{ pu}$$

Transformer, T₂

$$kV_{b \text{ old}} \frac{132}{11} = kV_{b \text{ new}}$$

$$kV_{b \text{ new}} = 132 \times \frac{11}{132}$$

$$kV_{b \text{ new}} = 11 \text{ kV}$$

$$Z_{pu, T_2} = 0.1 \times \left(\frac{20}{20}\right) \times \left(\frac{11}{11}\right)^2$$

$$Z_{pu, T_2} = j0.1 \text{ pu}$$

Load:-

$$Z_{pu, H} = 0.15 \times \left(\frac{20}{15}\right) \times \left(\frac{11}{11}\right)^2$$

$$Z_{pu, H} = j0.2 \text{ pu}$$

Sub:

Sub. Code:

Year/Sem:

Unit No.:

Session No.:

Date:

4. The rating of Single line diagram of the given below:-

Synchronous Generator:-

20 MVA, 11 kV, $x'' = 0.15 \text{ pu}$

Synchronous motor

15 MVA, 11 kV, $x'' = 0.15 \text{ pu}$

Transformer, T_1

25 MVA, $12.5/132 \text{ kV}$, $x = 0.1 \text{ pu}$


Transformer, T_2

20 MVA, $132/11 \text{ kV}$, $x = 0.1 \text{ pu}$

Line impedance: $200 + j500 \Omega$

Static load: 5 MVA, 0.8 pf lagging

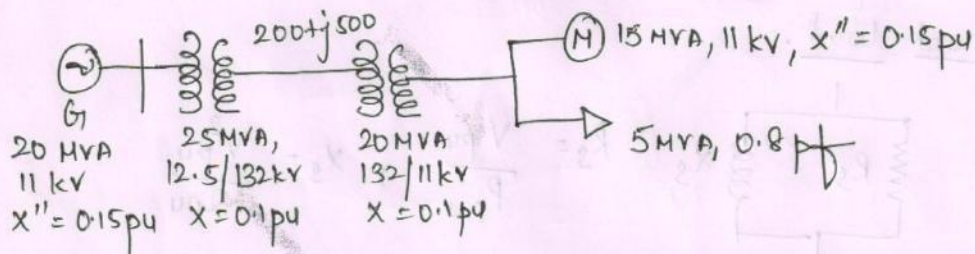Choose 132 kV, 20 MVA as base values on Transmission line



Sol:-

Transmission line, T_L

$$Z_{pu, T_L} = \frac{Z}{Z_b}$$

$$Z_b = \frac{(kVA)^2}{MVA} = \frac{(132)^2}{20} = 871.2 \Omega$$

$$Z_{pu, T_L} = \frac{Z}{Z_b} = \frac{200 + j500}{871.2} = 0.229 + j0.573$$

$$Z_{pu, T_L} = 0.229 + j0.573$$

Sub:

Sub. Code:

Year/Sem:

Unit No.:

Session No.:

Date:

Resistive load:-

$$Z_{pu, R} = \frac{Z}{Z_b}$$



$$= \frac{500}{Z_b}$$

$$Z_b = \frac{(210)^2}{100} = 441 \Omega$$

$$Z_b = 441 \Omega$$

$$Z_{pu, R} = \frac{j500}{441}$$

$$Z_{pu, R} = j1133 \text{ p.u.}$$

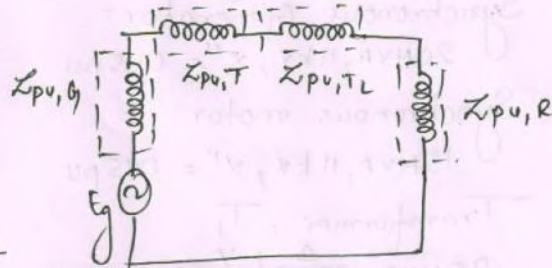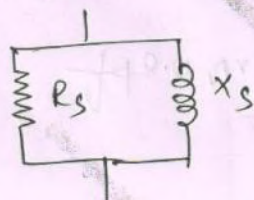Load Representation:-Shunt load:-

$$R_s = \frac{V_{pu}^2}{P_{pu}}, \quad X_s = \frac{V_{pu}^2}{Q_{pu}}$$

Series load

$$R_s = V_{pu}^2 \cdot S_b \cdot \frac{P}{P^2 + Q^2}$$

$$X_s = V_{pu}^2 \cdot S_b \cdot \frac{Q}{P^2 + Q^2}$$

Sub:

Sub. Code:

Year/Sem:

Unit No.:


Session No.:

Date:

Transformer T_3 :-

$$Z_{pu, T_3} = 0.1 \times \left(\frac{50}{35} \right) \times \left(\frac{220}{220} \right)^2$$

$$Z_{pu, T_3} = j0.142 pu$$

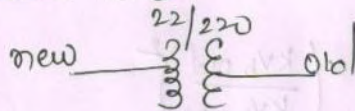
Generator, G_3 :-

$$KV_b \text{ new} = 220 \times \frac{22}{220}$$

$$KV_b \text{ new} = 22 kV$$

$$Z_{pu, G_3} = 0.2 \times \left(\frac{50}{30} \right) \times \left(\frac{20}{22} \right)^2$$

$$Z_{pu, G_3} = j0.275 pu$$

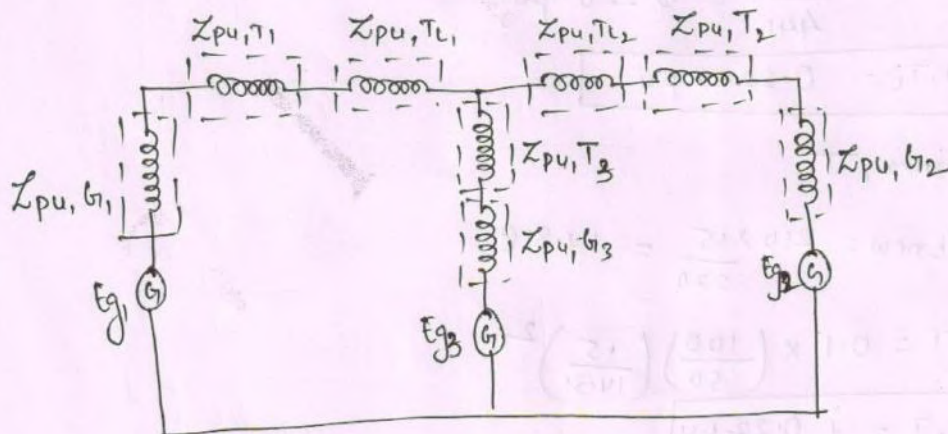

Sub:

Sub. Code:


Year/Sem:

Unit No.:

Session No.:

Date:

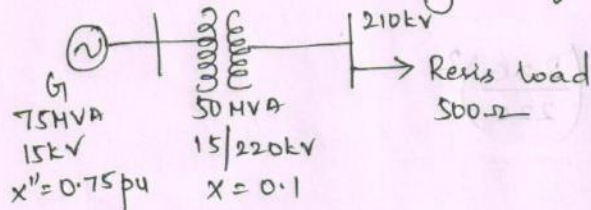3. Draw the impedance diagram of the given ckt



Assume 100 MVA & 210 kV in transmission line

Sol

$$Z_{pu, \text{new}} = Z_{pu, \text{old}} \times \left(\frac{\text{MVA}_{\text{new}}}{\text{MVA}_{\text{old}}} \right) \times \left(\frac{\text{KV}_{\text{b old}}}{\text{KV}_{\text{b new}}} \right)^2$$

Transmission line, T_L

$$Z_{pu, T_L} = \frac{Z}{Z_b}$$

$$Z_b = \frac{(\text{kVA})^2}{\text{MVA}} = \frac{(210)^2}{100} = 441 \Omega$$

$$Z_{pu, T_L} = \frac{100}{441} = 0.2267 \text{ pu}$$

$$Z_{pu, T_L} = 0.2267 \text{ pu}$$

Transformer, T

$$\text{KV}_{\text{b new}} = \frac{210 \times 15}{220} = 14.318$$

$$Z_{pu, T} = 0.1 \times \left(\frac{100}{50} \right) \left(\frac{15}{14.31} \right)^2$$

$$Z_{pu, T} = j 0.22 \text{ pu}$$

Generator, G

$$Z_{pu, G} = 0.75 \times \left(\frac{100}{75} \right) \left(\frac{15}{14.318} \right)^2$$

$$Z_{pu, G} = j 14 \text{ pu}$$

Sub:

Unit No.:

Sub. Code:

Session No.:

Year/Sem:

Date:

Transmission line, $T_L = j100 \Omega$

$$Z_{pu, T_L} = \frac{Z}{Z_b} = \frac{j100}{Z_b}$$

$$Z_b = \frac{(kV_b)^2}{MVA} = \frac{(220)^2}{50} = 968 \Omega$$

$$Z_{pu, T_L} = \frac{j100}{968}$$

$$Z_{pu, T_L} = j0.103 pu$$

$$\begin{aligned} Y \text{ connection, } V_p &= V_L / \sqrt{3} \\ V_L &= \sqrt{3} V_p \\ \Delta \text{ connection, } V_p &= V_L \end{aligned}$$


Transformer T_2 :-

$$30 MVA, \sqrt{3} \times 127 / 18 \text{ kV}, x = 0.1 pu$$

$$30 MVA, 220 / 18 \text{ kV}, x = 0.1 pu$$

$$Z_{pu, T_2} = 0.1 \times \left(\frac{50}{30} \right) \times \left(\frac{220}{220} \right)^2$$

$$Z_{pu, T_2} = j0.167 pu$$

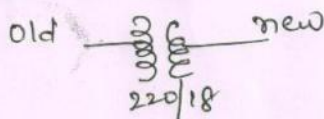Generator, G_2 :-

$$kV_{b, new} = 220 \times \frac{18}{220} = 18 \text{ kV}$$

$$Z_{pu, G_2} = 0.2 \times \left(\frac{50}{30} \right) \times \left(\frac{18}{18} \right)^2$$

$$Z_{pu, G_2} = j0.333 pu$$

Sub:

Sub. Code:

Year/Sem:

Unit No.:

Session No.:

Date:

Draw the impedance diagram with all the reactance marked in per unit choose a base of 50 MVA, 13.8 kV

Sol:- $Z_{pu, new} = Z_{pu, old} \times \frac{MVA_{b, new}}{MVA_{b, old}} \times \left[\frac{KV_{b, old}}{KV_{b, new}} \right]^2$

$$MVA_b = 50 \text{ MVA}$$

$$KV_b = 13.8 \text{ kV}$$

Generator 1:-

$$Z_{pu, G1, new} = \frac{220}{500} \times 0.2 \times \frac{50}{20} \times \left[\frac{13.8}{13.8} \right]^2$$


$$Z_{pu, G1} = j0.5 \text{ pu}$$

Transformer 1:-

$$Z_{pu, T1, new} = 0.2 \times \frac{50}{25} \times \left[\frac{13.8}{13.8} \right]^2$$

$$Z_{pu, T1} = j0.4 \text{ pu}$$

Transmission Line, T_L — $j80 \Omega$

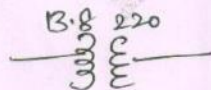

$$KV_{b, new} = 13.8 \times \left[\frac{220}{13.8} \right]$$

$$KV_{b, new} = 220 \text{ kV}$$

$$Z_{pu, T_L} = \frac{Z}{Z_b} = \frac{j80}{Z_b}$$

$$Z_b = \frac{(KV_b)^2}{MVA} = \frac{(220)^2}{50}$$

$$Z_b = 968 \Omega ; Z_{pu, T_L} = \frac{j80}{968} = j0.082, Z_{pu, T_L} = j0.082$$

Sub:

Sub. Code:

Year/Sem:

Unit No.:

Session No.:

Date:

Motor:- M:-


$$KV_{bnew} = KV_{b old} \times \frac{LV}{HV}$$

$$= 200 \times 20 / 200$$

$$KV_{bnew} = 20 \text{ kV}$$

$$Z_{pu, M} = 0.08 \times \left(\frac{100}{43.2} \right) \times \left(\frac{18}{20} \right)^2$$

$$Z_{pu, M} = j0.15 \text{ pu}$$

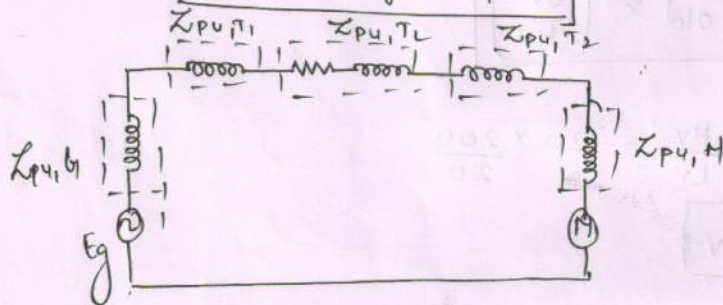

- ②. The one line diagram of a unloaded power system which is shown in the fig below. Reactance on two section of Tr. line are shown in the diagram. The generators and T/t are rated below:-

G_1 : 20 MVA, 13.8 kV, $x'' = 0.2 \text{ pu}$

G_2 : 30 MVA, 18 kV, $x'' = 0.2 \text{ pu}$


G_3 : 30 MVA, 20 kV, $x'' = 0.2 \text{ pu}$

T_1 : 25 MVA, 13.8/220 kV, $x'' = 0.2 \text{ pu}$

T_2 : 3, ^{single} units each, rated

10 MVA, 127/18 kV, $x = 10\%$.

T_3 : 35 MVA, 220/20 kV, $x = 10\%$.

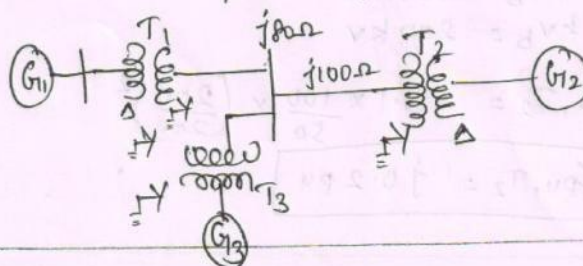

Sub:

Sub. Code:

Year/Sem:


Unit No.:

Session No.:


Date:

Transmission line:-

Change of KV base of transformer

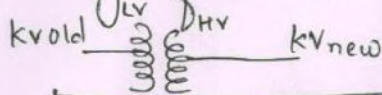
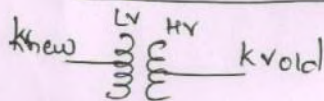
$$KV_{b\text{ new}} = KV_{b\text{ old}} \times \left[\frac{HV}{LV} \right]$$



$$KV_{b\text{ new}} = KV_{b\text{ old}} \times \left[\frac{LV}{HV} \right]$$

$$KV_{b\text{ new}} = KV_{b\text{ old}} \times \frac{HV}{LV} = 20 \times \frac{200}{20}$$

$$KV_{b\text{ new}} = 200 \text{ kV}$$

$$Z_{pu} = \frac{Z}{Z_b} = \frac{120 + j200}{Z_b}$$

$$Z_b = \frac{KV_b^2}{MVA_b} = \frac{(200)^2}{100}$$

$$Z_b = 400$$

$$= \frac{120 + j200}{400}$$

$$Z_{pu, T_1} = 0.3 + j0.5 \text{ pu}$$

Transformer, T₂:-

$$MVA_b = 100 \text{ MVA}$$

$$KV_b = 200 \text{ kV}$$

$$Z_{pu, T_2} = 0.1 \times \frac{100}{50} \times \left(\frac{200}{200} \right)^2$$

$$Z_{pu, T_2} = j0.2 \text{ pu}$$

Sub:

Sub. Code:


Year/Sem:

Unit No.:

Session No.: 07/08

Date:

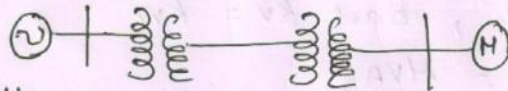1. 3 ϕ power and line - line voltage rating of a electrical power system is shown below



$$G_1 = 60 \text{ MVA}, 20 \text{ kV}, x'' = 9\% = 0.09$$


$$T_1 = 50 \text{ MVA}, 20/200 \text{ kV}, x = 10\% = 0.1$$

$$T_2 = 50 \text{ MVA}, 200/20 \text{ kV}, x = 10\% = 0.1$$

$$M = 43.2 \text{ MVA}, 18 \text{ kV}, x'' = 8\% = 0.08$$

$$\text{Line} = 200 \text{ kV}, Z = 120 + j200 \Omega$$

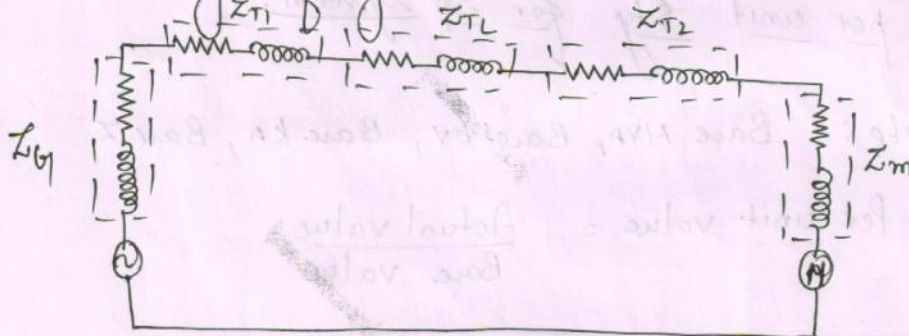Draw the impedance diagram showing all impedance in per unit on a 100 MVA base, choose 20 kV has a base voltage of generator.



$$Z_{pu, \text{new}} = Z_{pu, \text{old}} \times \left[\frac{\text{MVA}_{b, \text{new}}}{\text{MVA}_{b, \text{old}}} \right] \times \left[\frac{\text{kV}_{b, \text{old}}}{\text{kV}_{b, \text{new}}} \right]^2$$

old - given value
new - assume value

Let

$$\text{MVA}_b = 100 \text{ MVA}, \text{kV}_b = 20 \text{ kV}$$

Generator:-

$$Z_{pu, G, \text{new}} = 0.09 \times \left[\frac{100}{60} \right] \times \left[\frac{20}{20} \right]^2$$

$$Z_{pu, G, \text{new}} = j0.15 \text{ pu}$$

Transformer:-

$$Z_{pu, T, \text{new}} = 0.1 \times \left[\frac{100}{50} \right] \times \left[\frac{20}{20} \right]^2$$

$$Z_{pu, T, \text{new}} = j0.2 \text{ pu}$$

Sub:
Sub. Code:
Year/Sem:

Unit No.:
Session No.:
Date:

Here,

Base value of power & voltage are assumed

Base MVA = MVA_b , Base KV = KV_b

Base current, $KVA_b = \frac{MVA_b}{KV_b}$

Base impedance, $Z_b = \frac{KV_b}{KA_b}$

Base impedance = $\frac{KV_b}{MVA_b} = \frac{KV_b}{MVA_b} \times KV_b$

from the above base value, the per unit value of power, voltage, current & impedance can be found.

Calculations of per unit Qty for 3 ϕ system:-

To calculate: Base MVA, Base KV, Base KA, Base Z

WKT :- Per unit value = $\frac{\text{Actual value}}{\text{Base value}}$

Here:-

$$\text{Base } MVA_b / P_h = \frac{MVA_b}{3}$$

$$\text{Base Volt } (KV_b) / P_h = \frac{KV_b}{\sqrt{3}}$$

$$\text{Base current } (KA_b) / P_h = \frac{MVA_b / 3}{\frac{KV_b}{\sqrt{3}}}$$

$$\text{Base impedance } / P_h = Z_b = \frac{(\frac{KV_b}{\sqrt{3}})^2}{\frac{MVA_b}{3}} = \frac{KV_b^2}{MVA_b}$$

$$Z_{ph \text{ new}} = Z_{ph \text{ old}} \times \left(\frac{MVA_{b \text{ new}}}{MVA_{b \text{ old}}} \right) \times \left(\frac{KV_{b \text{ old}}}{KV_{b \text{ new}}} \right)^2 \quad \text{old-given value}$$

Per Unit Representation:-

$$\text{Per unit} = \frac{\text{Actual value}}{\text{Base value}}$$

Advantage:-

- 1) The per unit impedances refer to both primary & secondary phase of transformer are the same.
- 2) The per unit impedances refer to both primary and secondary
- 3) Choice of confusion b/w line Qty & phase Qty greatly reduce.
- 4) The manufacture data is used to given in data
- 5) The computation effect is greatly reduce in per unit.

Calculation of per unit Qty for 1 ϕ system:-Parameters:-

- i) Power, $P = \text{MVA}_b$
- ii) Voltage, $V = \text{KV}_b$
- iii) Current, $I = \text{KA}_b$
- iv) Impedance, $Z = Z_b$

To calculate:-

Base MVA, Base KV, Base KA, Base Z

Wke:-

$$\text{Per unit value} = \frac{\text{Actual value}}{\text{Base value}}$$


Sub:
Sub. Code:
Year/Sem:

Unit No.:
Session No.: 06
Date:

Synchronous Motor Load:-

In motoring operation of Synchronous machine that current I_a is reverse so that voltage equation is

$$E = V_t - I_a Z_s$$

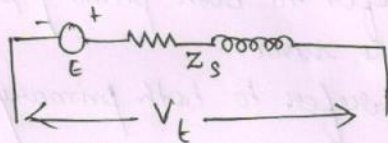


Here synchronous motor load is represented in same way as synchronous generator.

Induction Motor Load:-

For transient and steady state condition induction motors are neglected the stator current becomes zero.

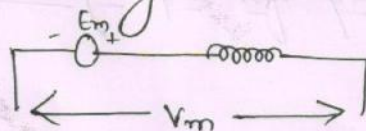Induction motor load is considered in fault current calculation during subtransient condition.



X_d'' = Sub transient reactance of I.M

3) Transmission Line Representation:-


* It is represented by its resistance, inductance and capacitance.

* There are two types of Transmission line they are


* T Method

* π Method

π -Method:-

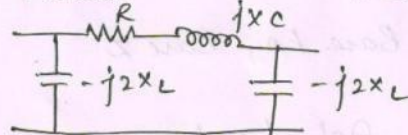

T-Method:-

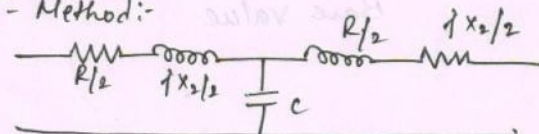

Sub:

Sub. Code:

Year/Sem:

Unit No.:

Session No.:

Date:

3) Modelling of Loads:-


- * Loads are composite in nature consisting of industrial & domestic load.
- * Industrial load consists of large 3 ϕ motor.
- * Domestic load consists of lighting, heating & 1 ϕ devices.

Representation of load:-

(Passive load no rotating)

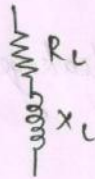a) Constant impedance representation:-

- * used in stability
- * load impedance is calculated as follows:-



$$Z_L = V/I$$

$$\text{WKT, } S = P + jQ = VI^*$$

$$S^* = P - jQ = V^* I$$

$$I = \frac{P - jQ}{V^*}$$

$$\therefore Z_L = \frac{V}{\frac{P - jQ}{V^*}}, \quad Z_L = \frac{V^2}{P - jQ}$$

b) Constant power representation:-

- * used in transient stability.
- * Here passive loads are represented by constant active & reactive components.

c) Constant current representation:-

- * Transient stability analysis use constant current representation

$$\text{load current, } I_L = \frac{P - jQ}{V^*}, \quad I_L = I \angle \delta - \theta$$

where $\theta = \tan^{-1} Q/P$ - power factor angle

Sub:

Sub. Code:

Year/Sem:


Unit No.:

Session No.: 05


Date:

2) Modelling of Transformer:


Equivalent Ckt of transformer:

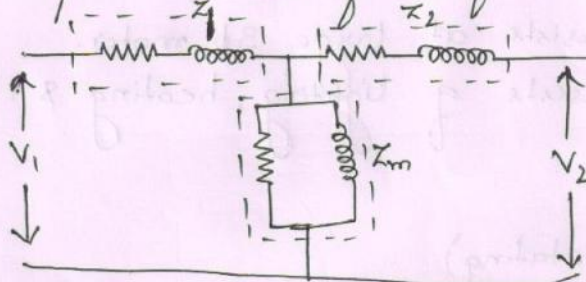a) Power flow Studies:

Here the shunt impedance its magnetising in nature it affect its neglected in power flow. Here transformer are model by series leakage reactance as shown.

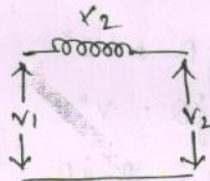b) Short Circuit Studies:

Here also magnetising impedance are neglected. Model of transformer is the reactance only.

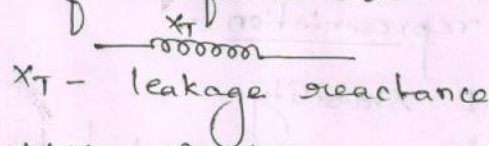c) Stability Studies:

Here transformer are modelled by series reactance which is leakage reactance.

Sub:

Unit No.:

Sub. Code:

Session No.:

Year/Sem:

Date:

$$Z_{11} = 0.753j - \frac{0.158j \times 0.158j}{0.673j}, Z_{11, \text{new}} = 0.715j$$

$$Z_{12} = 0.654j - \frac{0.158j \times 0.19j}{0.673j}, Z_{12, \text{new}} = 0.609j$$

$$Z_{13} = 0.496j - \frac{(0.158j \times 0.158j)}{0.673j} = Z_{13, \text{new}} = 0.533j$$

$$Z_{14} = 0.496j - \frac{0.158j \times (-0.358j)}{0.673j}, Z_{14, \text{new}} = 0.580j$$

$$Z_{21, \text{new}} = 0.609j$$

$$Z_{22, \text{new}} = 0.785j - \frac{(0.19j \times 0.19j)}{0.673j}, Z_{22, \text{new}} = 0.731j$$

$$Z_{23, \text{new}} = 0.595j - \frac{(0.49j \times (-0.158j))}{0.673j}, Z_{23, \text{new}} = 0.639j$$

$$Z_{24, \text{new}} = 0.595j - \frac{(0.19j) \times (-0.358j)}{0.673j}, Z_{24, \text{new}} = 0.696j$$

$$Z_{31, \text{new}} = 0.533j, Z_{32, \text{new}} = 0.639j,$$

$$Z_{33, \text{new}} = 0.753j - \frac{(0.158j \times 0.158j)}{0.673j}, Z_{34, \text{new}} = 0.668j$$

$$Z_{41, \text{new}} = 0.580j, Z_{42, \text{new}} = 0.696j, Z_{43, \text{new}} = 0.668j$$

$$Z_{44, \text{new}} = 0.953j - \frac{(-0.358j) \times (-0.358j)}{0.673j}, Z_{44, \text{new}} = 0.7625j$$

$$Z_{\text{bus, new}} = \begin{bmatrix} 0.715j & 0.609j & 0.533j & 0.580j \\ 0.609j & 0.731j & 0.639j & 0.696j \\ 0.533j & 0.639j & 0.715j & 0.668j \\ 0.580j & 0.696j & 0.668j & 0.762j \end{bmatrix}$$

Sub:

Sub. Code:

Year/Sem:

Unit No.:


Session No.:

Date:

$$Z_{bus} = \begin{bmatrix} 0.754j & 0.654j & 0.496j \\ 0.654j & 0.785j & 0.595j \\ 0.496j & 0.595j & 0.753j \end{bmatrix}$$

Step 5

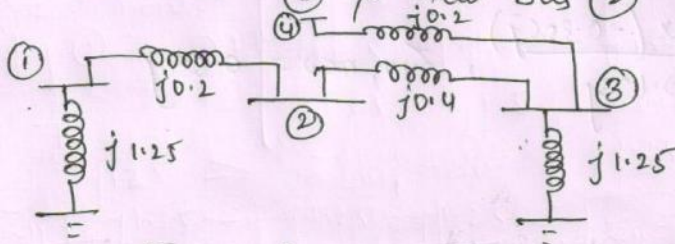
Addition of branch of impedance, $j = 0.2$ in b/w old bus ③ & new bus ②



$$Z_{bus} = \begin{bmatrix} 0.754j & 0.654j & 0.496j & 0.496j \\ 0.654j & 0.785j & 0.595j & 0.595j \\ 0.496j & 0.595j & 0.753j & 0.753j \\ 0.496j & 0.595j & 0.753j & 0.953j \end{bmatrix}$$

Step 6:-

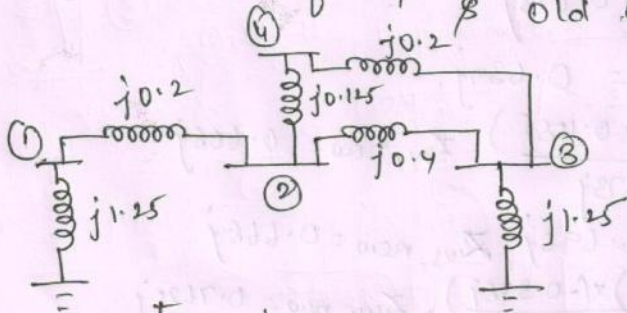Addition of impedance, $j0.125$ in b/w the old bus ④ & old bus ②.



$$Z_{bus} = \begin{bmatrix} 0.754j & 0.654j & 0.496j & 0.496j & 0.158j \\ 0.654j & 0.785j & 0.595j & 0.595j & 0.19j \\ 0.496j & 0.595j & 0.753j & 0.753j & -0.158j \\ 0.496j & 0.595j & 0.753j & 0.953j & -0.358j \\ 0.158j & 0.19j & -0.158j & -0.358j & 0.673j \end{bmatrix}$$

Sub:

Sub. Code:


Year/Sem:

Unit No.:

Session No.:

Date:

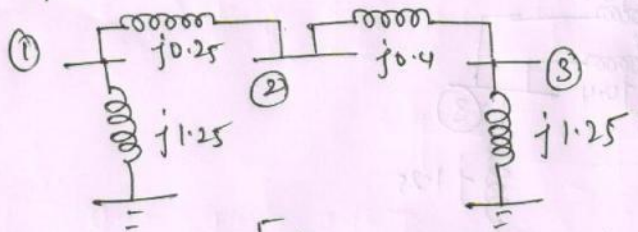Step ④ :- Add the impedance $z=j1.25$ b/w bus ③ & ref bus



$$Z_{bus, new} = \begin{bmatrix} j1.25 & j1.25 & j1.25 & j1.25 \\ j1.25 & j1.5 & j1.5 & j1.5 \\ j1.25 & j1.5 & j1.9 & j1.9 \\ j1.25 & j1.5 & j1.9 & j3.15 \end{bmatrix}$$

$$Z_{11} = j1.25 - \frac{j1.25 \times j1.25}{j3.15}, \quad \boxed{Z_{11} = 0.754j}$$

$$Z_{12} = j1.25 - \frac{j1.25 \times j1.5}{j3.15}, \quad \boxed{Z_{12} = 0.654j}$$

$$Z_{13} = j1.25 - \frac{j1.25 \times j1.9}{j3.15}, \quad \boxed{Z_{13} = 0.496j}$$

$$Z_{22} = 1.5j - \frac{1.5j \times 1.5j}{3.15j}, \quad \boxed{Z_{22} = 0.785j}$$


$$Z_{23} = 1.5j - \frac{1.5j \times 1.9j}{3.15j}, \quad \boxed{Z_{23} = 0.595j}$$

$$Z_{33} = 1.9j - \frac{1.9j \times 1.9j}{3.15j}, \quad \boxed{Z_{33} = 0.753j}$$

Sub:
Sub. Code:
Year/Sem:

Unit No.:
Session No.:
Date:

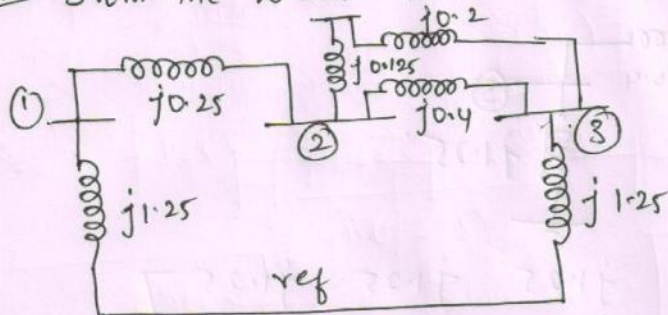Prob From the Z_{bus} - matrix the Ckt shown below



Step ① :- Add the impedance, $Z = j1.25$ b/w ref bus & bus ①

$$\begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} j1.25 \Rightarrow Z_{bus, new} = \begin{bmatrix} j1.25 \end{bmatrix}$$

Step ② :- Add the impedance $Z = j0.25$ b/w bus ① & bus ②

$$\begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} j1.25 \quad \begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} j0.25 \quad \begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} j1.25 \Rightarrow Z_{bus, new} = \begin{bmatrix} j1.25 & j1.25 \\ j1.25 & j1.5 \end{bmatrix}$$

Step ③ :- Add the impedance, $Z = j0.4$, b/w bus ② & bus ③

$$\begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} j1.25 \quad \begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} j0.25 \quad \begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} j0.4 \quad \begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} j1.25 \Rightarrow Z_{bus(3), new} = \begin{bmatrix} j1.25 & j1.25 & j1.25 \\ j1.25 & j1.5 & j1.5 \\ j1.25 & j1.5 & j1.9 \end{bmatrix}$$

Sub:

Sub. Code:

Year/Sem:

Unit No.:

Session No.:

Date:

$$Z_{21} = Z_{12} = j0.5$$

$$Z_{22} = j1.25 - \frac{(j1.25 \times j1.25)}{j1.25}, \quad Z_{22} = j0.625$$

$$Z_{23} = j1.25 - \frac{(j1.25 \times j1.25)}{j2.5}$$

$$Z_{23} = j0.625$$

$$Z_{31} = Z_{13} = j0.5$$

$$Z_{32} = Z_{23} = j0.625$$

$$Z_{33} = j1.3 - \frac{(j1.25 \times j1.25)}{j2.5}$$

$$Z_{33} = j0.675$$

$$Z_{bus} = \begin{bmatrix} 0.6j & j0.5 & 0.5j \\ 0.5j & j0.625 & j0.625 \\ j0.5 & j0.625 & j0.675 \end{bmatrix}$$